
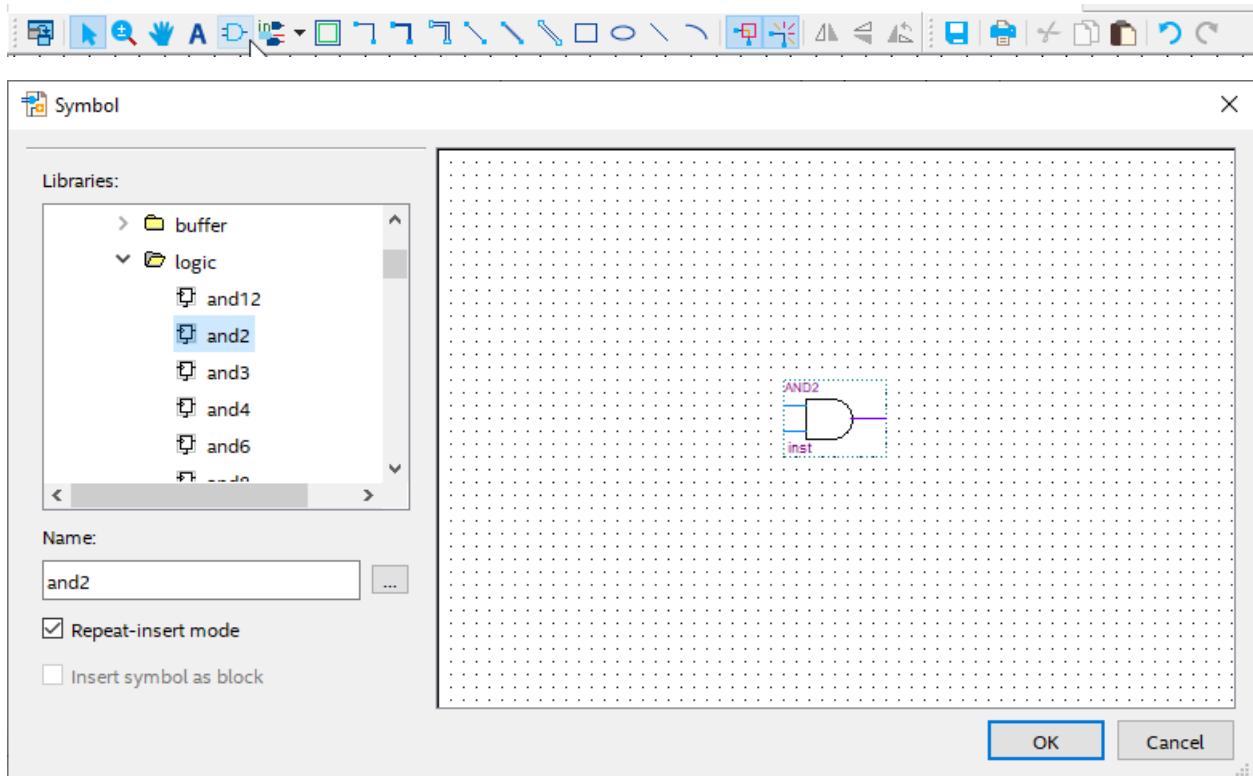


ZHANG_CHUE


Task 2: "2:1 Mux"

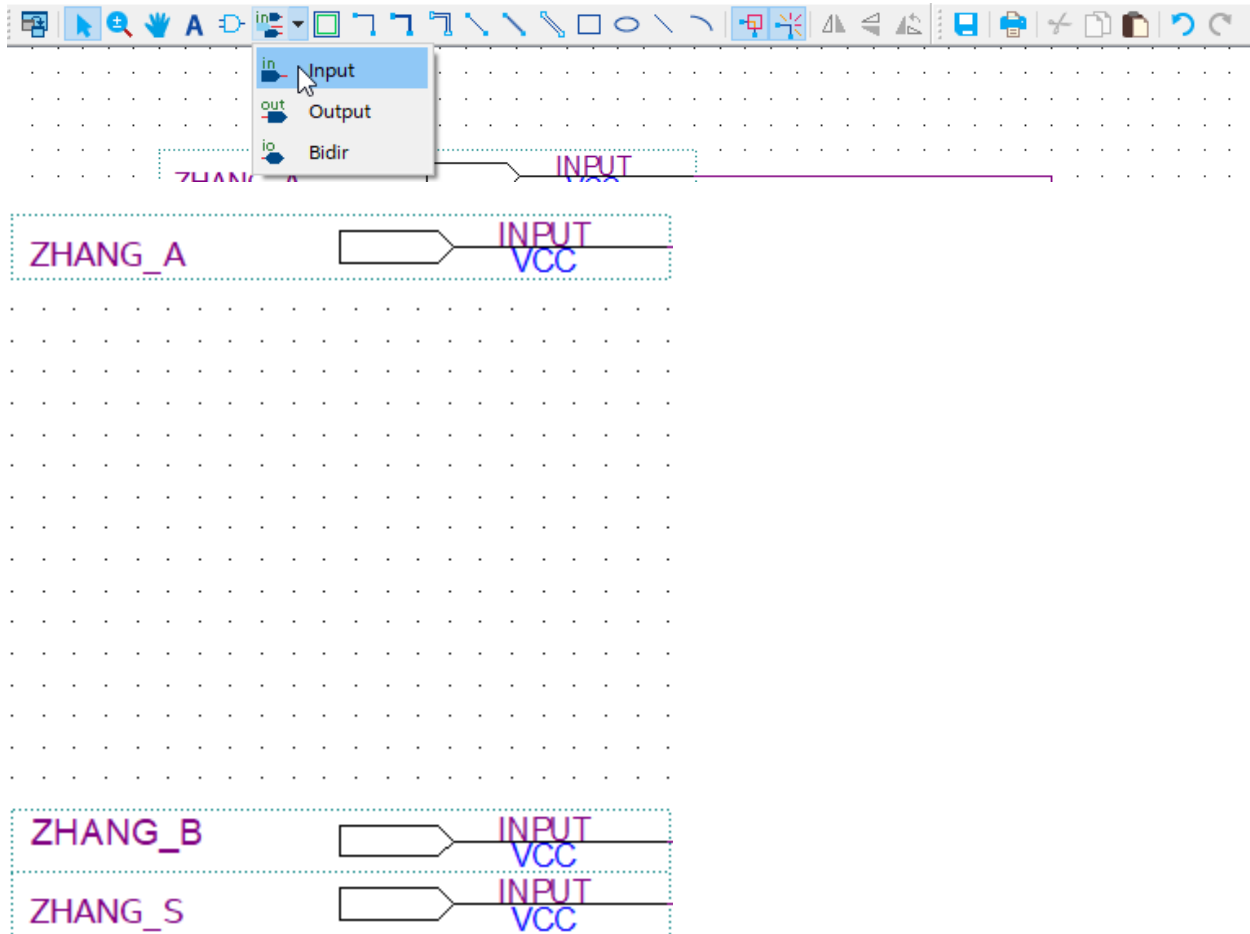


Next, I go to the pins tool dropdown menu and select input. For the MUX, I used 3 inputs



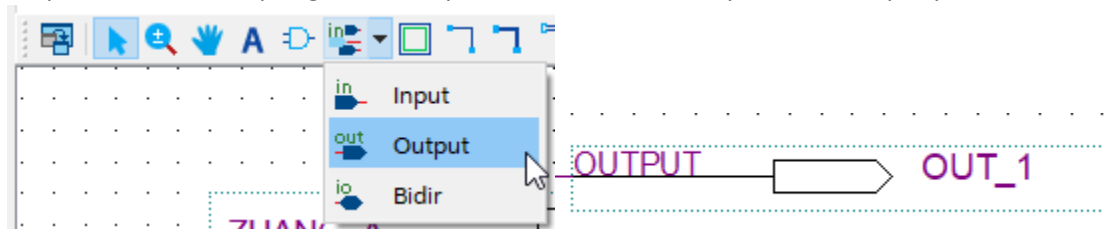
I repeat the same steps again for output Pins, however, I only use one output pin



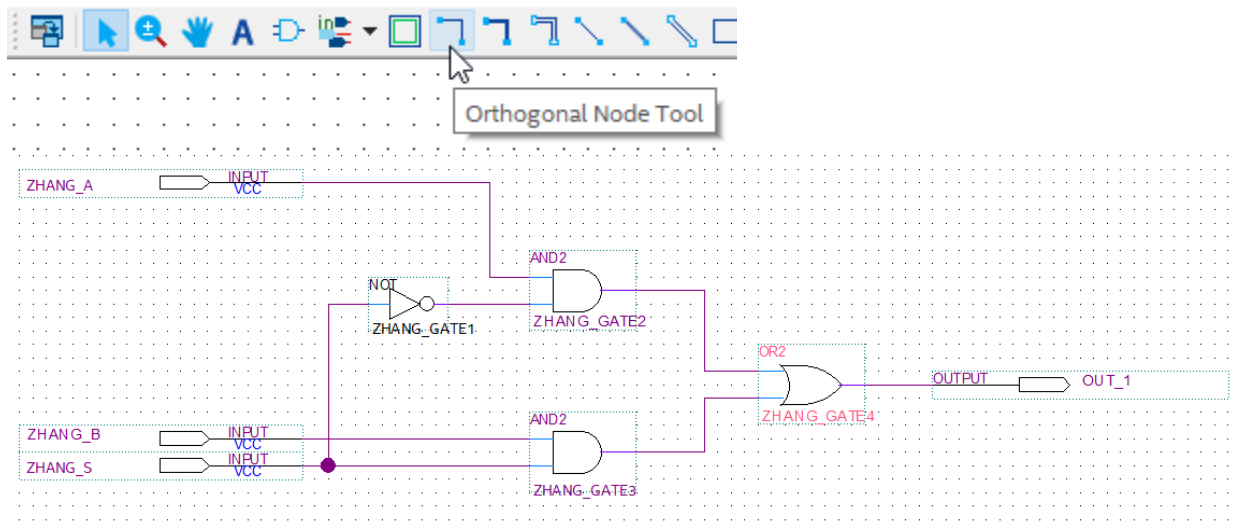
Then I use the Orthogonal Node tool to connect the inputs and outputs to the gates.






In the figure above, what is shown is a 2:1 MUX where we have 3 inputs. Input A, Input B and a Selector input. The selector is inputted in the NOT-gate which is then inputted in the ZHANG_GATE2 with ZHANG_A input. It is also inputted into the ZHANG_GATE3 with ZHANG_B input and finally both ZHANG_GATE2 and ZHANG_GATE3 and inputted together into ZHANG_GATE4 (OR-gate) where the result will be outputted.

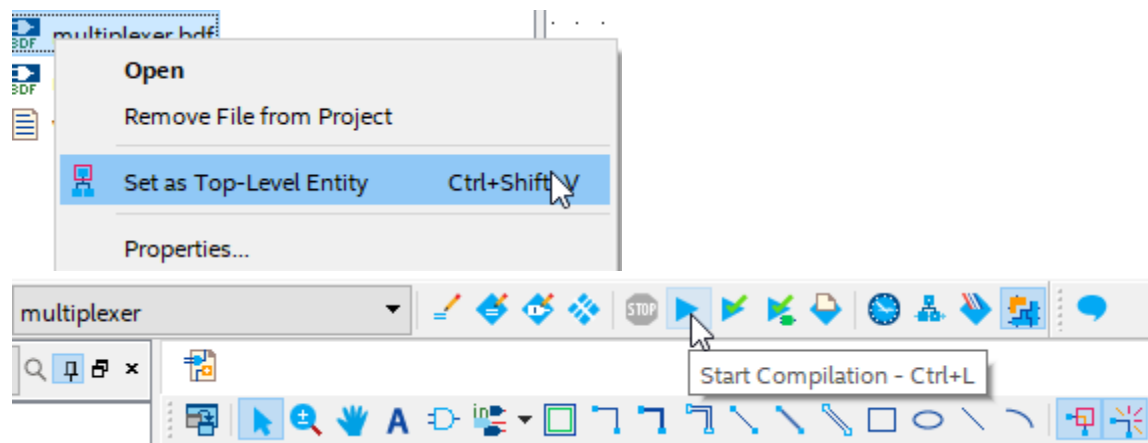


Flow Summary	
 <<Filter>>	
Flow Status	Successful - Mon Aug 30 12:47:16 2021
Quartus Prime Version	20.1.1 Build 720 11/11/2020 SJ Lite Edition
Revision Name	multiplexer
Top-level Entity Name	multiplexer_symbol
Family	Cyclone V
Device	5CGXFC7C7F23C8
Timing Models	Final
Logic utilization (in ALMs)	1 / 56,480 (< 1 %)
Total registers	0
Total pins	4 / 268 (1 %)
Total virtual pins	0
Total block memory bits	0 / 7,024,640 (0 %)
Total DSP Blocks	0 / 156 (0 %)
Total HSSI RX PCSs	0 / 6 (0 %)
Total HSSI PMA RX Deserializers	0 / 6 (0 %)
Total HSSI TX PCSs	0 / 6 (0 %)
Total HSSI PMA TX Serializers	0 / 6 (0 %)
Total PLLs	0 / 13 (0 %)
Total DLLs	0 / 4 (0 %)

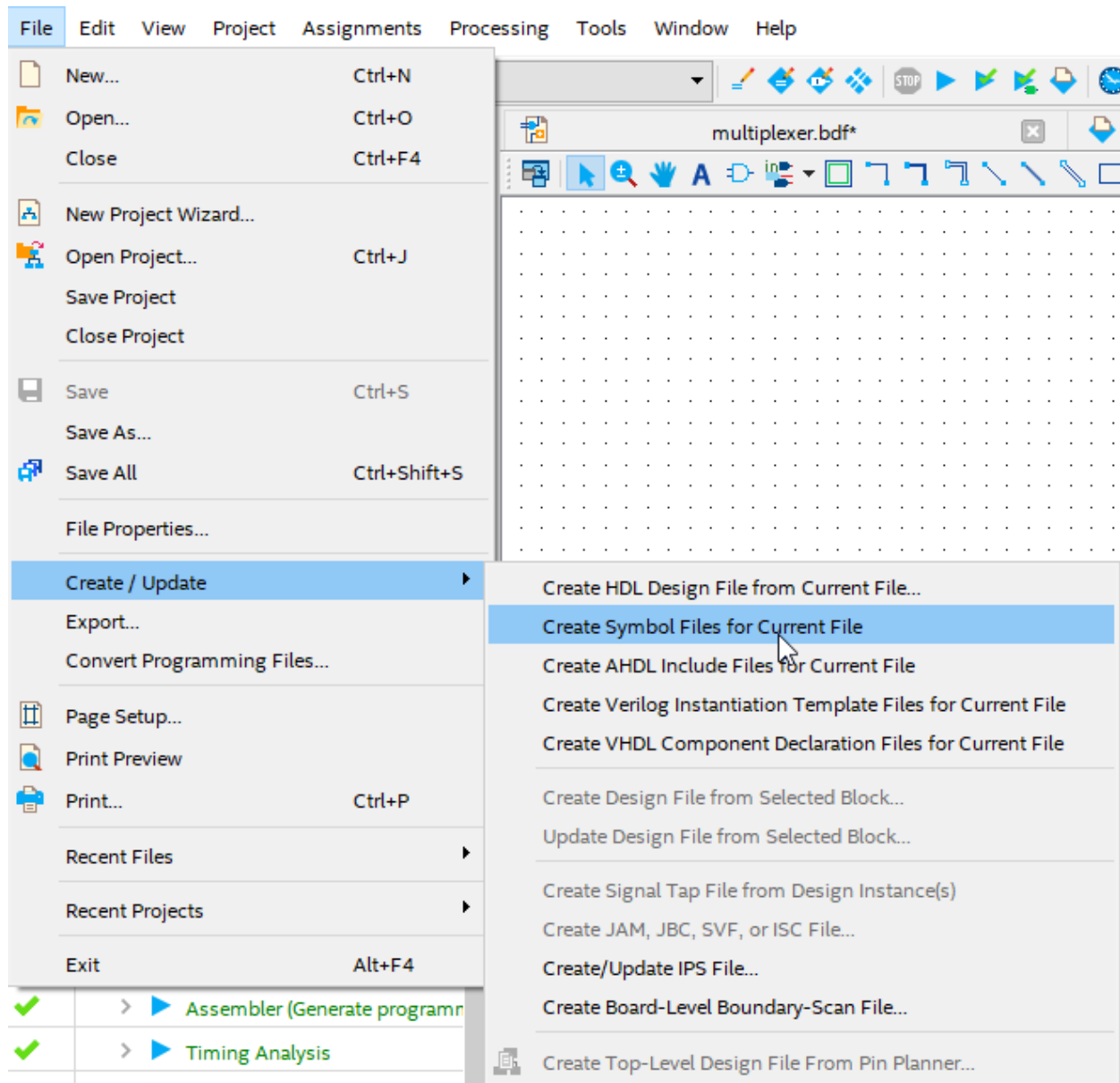In this next few screenshot, what I did was I set the MUX bdf file to top level where I then compile to ensure that everything is working properly.




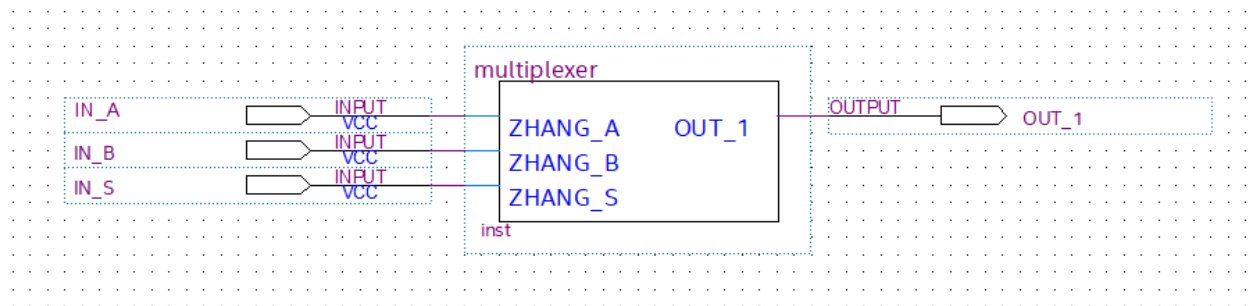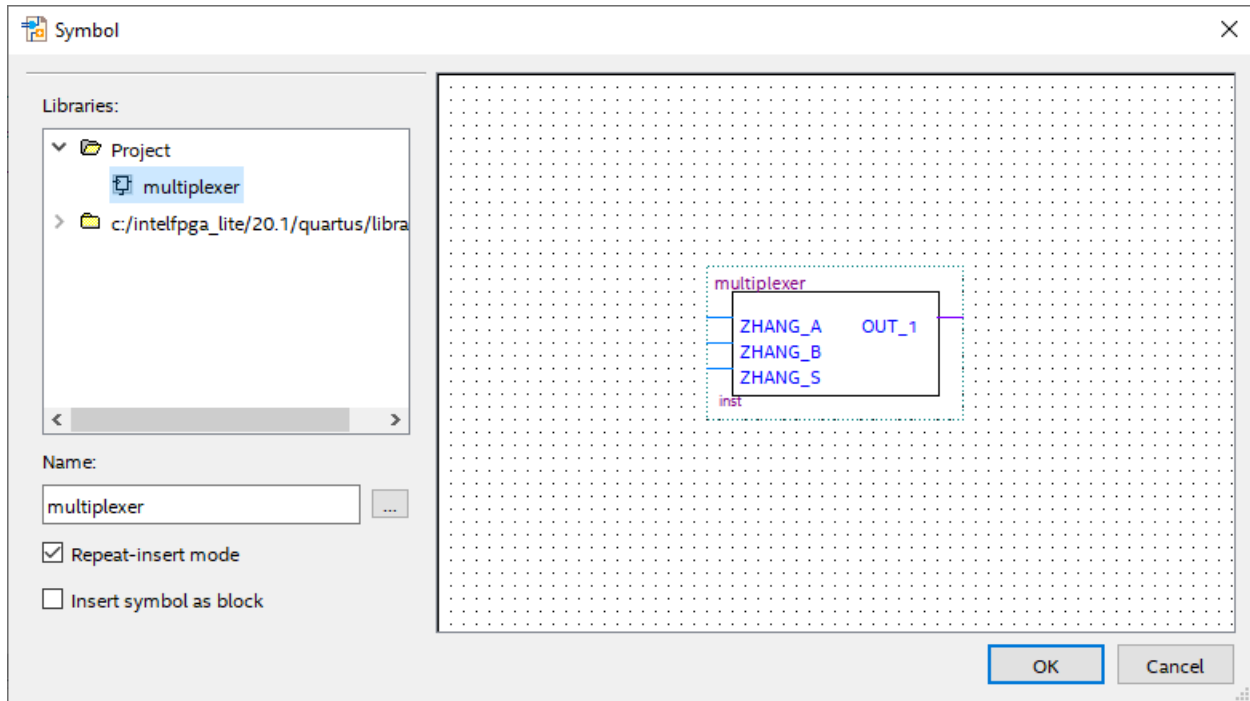

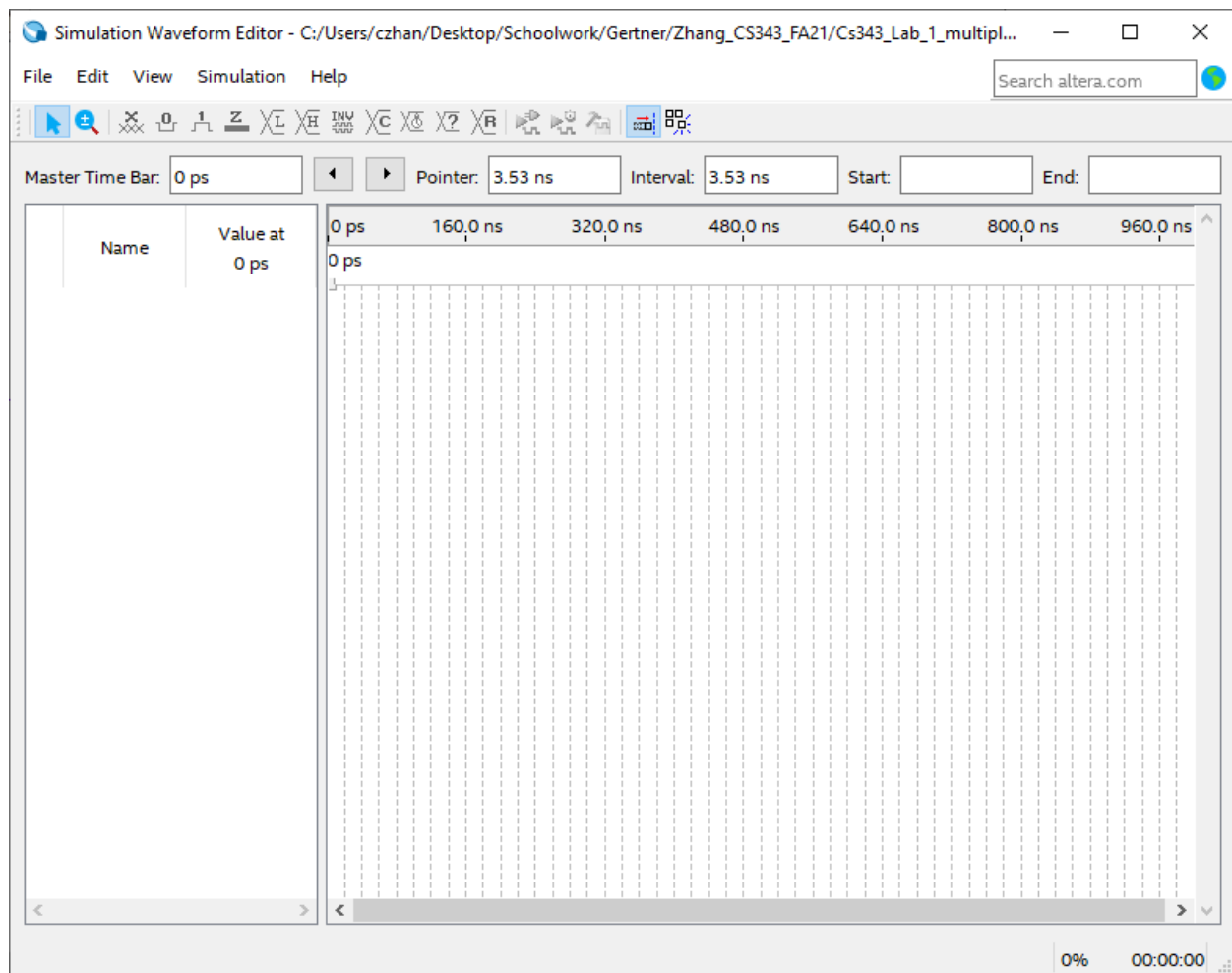
Next, I create a symbol file for the current file and in another block design file, I go into the symbols tool in the project dropdown, I can see the design for my 2:1 MUX. I press OK and put it in the new block design file with 3 inputs and 1 output under the names of IN_A, IN_B, IN_S, OUT_1 Respectively.



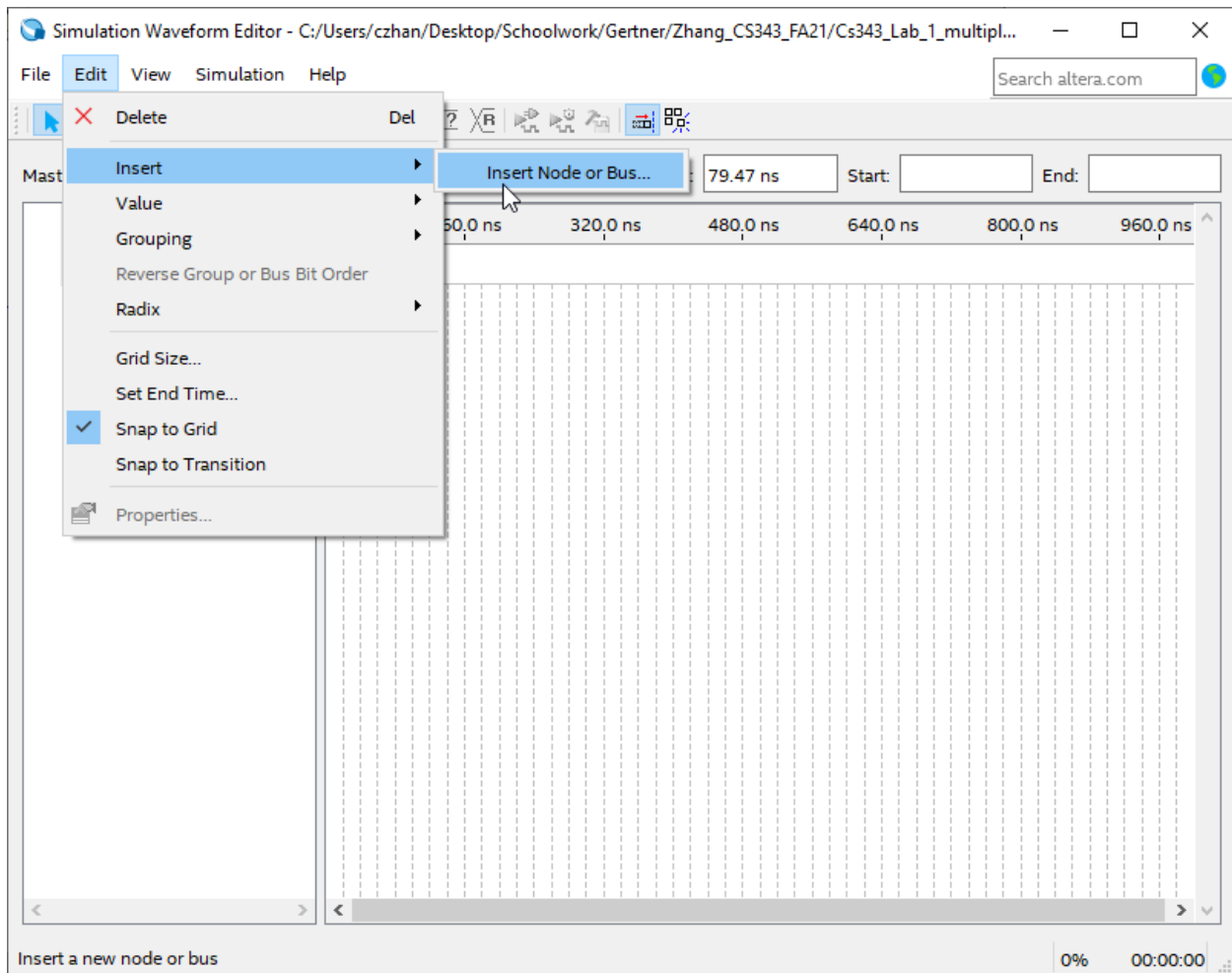I make a new "University Program VWF" file



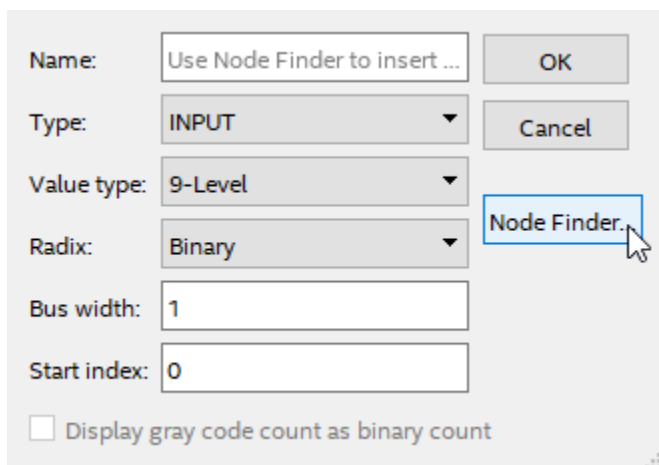I press Edit -> Insert -> Insert Node or Bus and a pop up should show up.



In the popup, press Node Finder and another popup should show up

Named: Filter: Pins: all OK

Look in: ... List Cancel

Nodes Found:

Name	Type
------	------

Selected Nodes:





Name	Type
------	------

> >> < << Start node search





Named: Filter: Pins: all OK

Look in: ... List Cancel

Nodes Found:


Name	Type
 IN_A	Input
 IN_B	Input
 IN_S	Input
 OUT_1	Output

Selected Nodes:


Name	Type
 IN_A	Input
 IN_B	Input
 IN_S	Input
 OUT_1	Output

> >> < <<

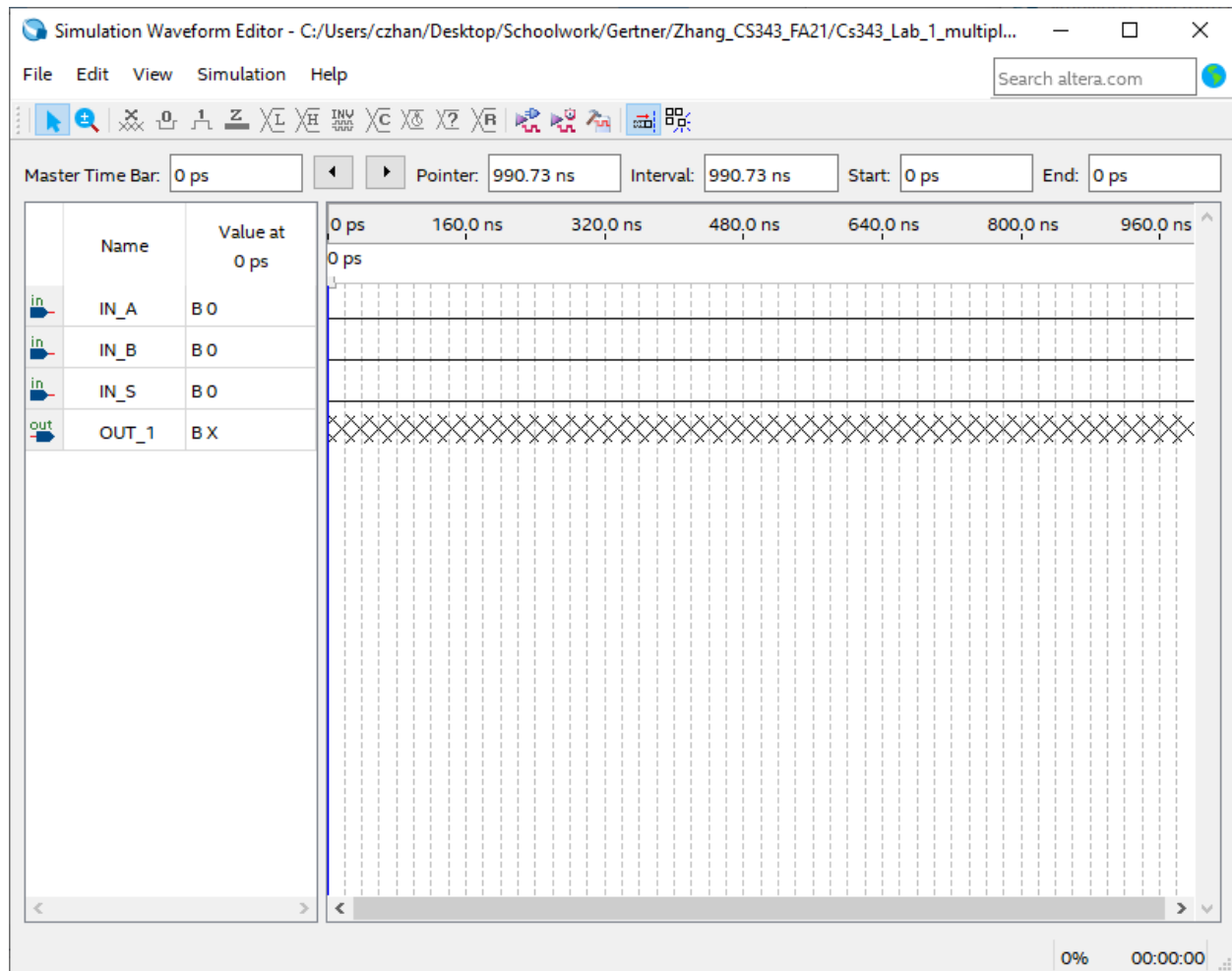In the new popup, press list and a list on the left with all inputs and outputs should show up, then press the >> symbol to select all nodes and press OK.



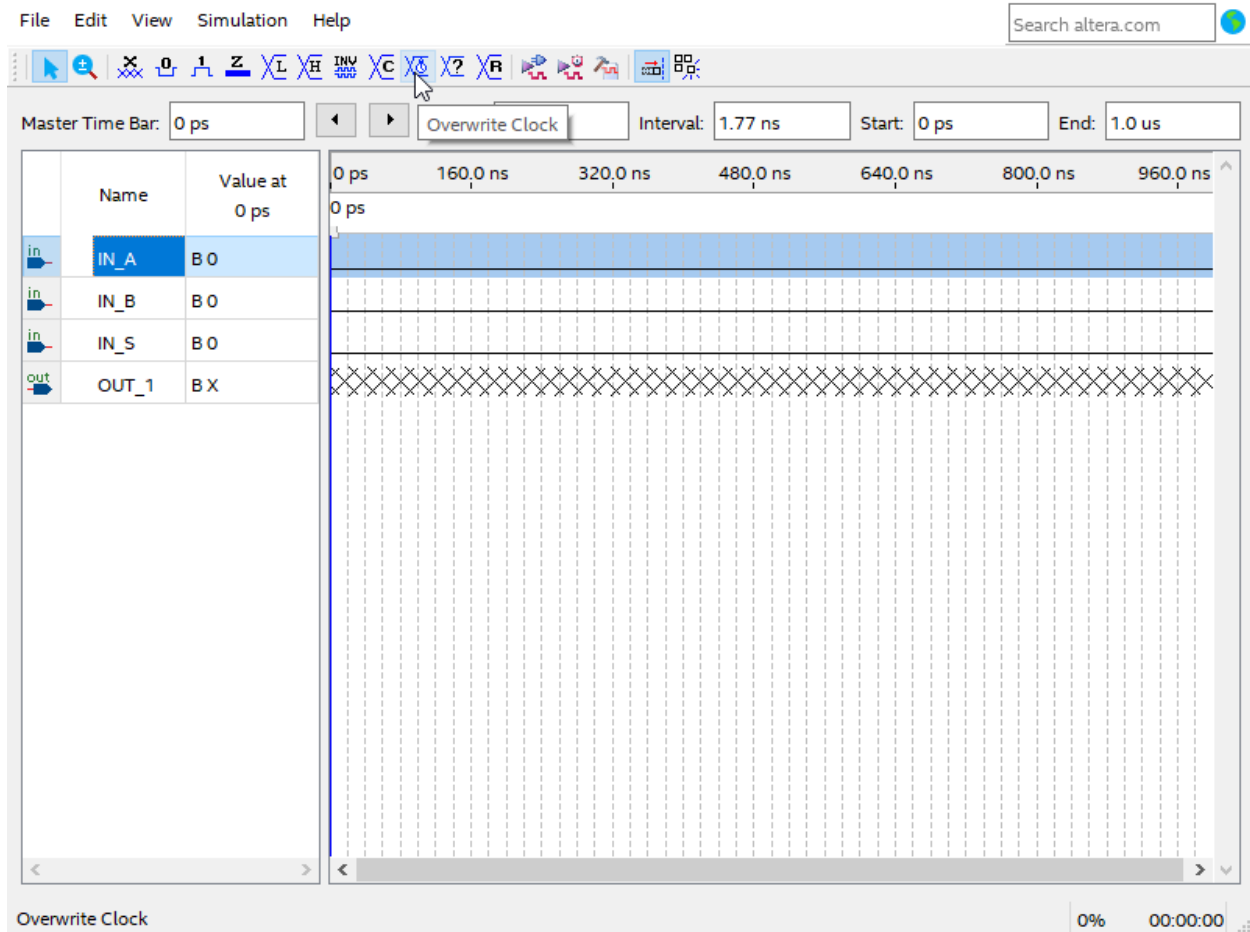This is what you should see and next I will start manually inputting values for the inputs so that we can generate the appropriate output for the MUX.



In the same file, I press on IN_A -> overwrite Clock symbol which allows me to change the values of the input at a set interval. (A POPUP SHOULD SHOW UP)


Clock [X]

Base waveform on time period


Period: ns

Offset: ns

Duty cycle (%):


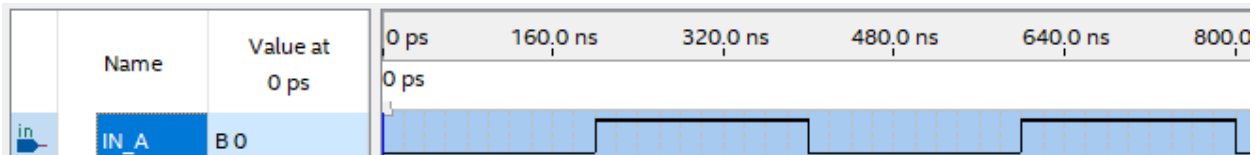


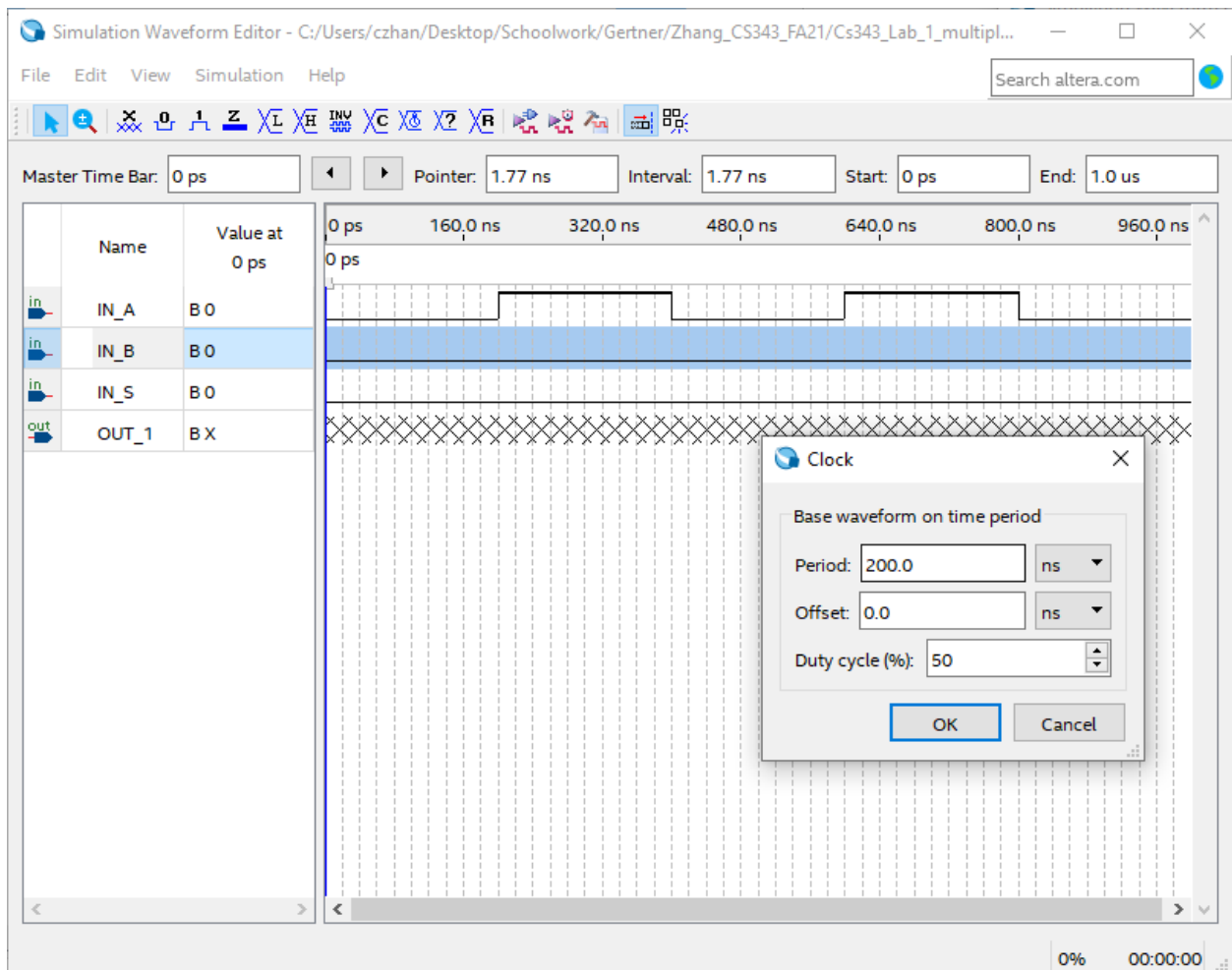In the popup window, I set the period to 400 ns which makes it so that the value is at 1 at 200ns-400ns and 1 at 600ns-800ns.






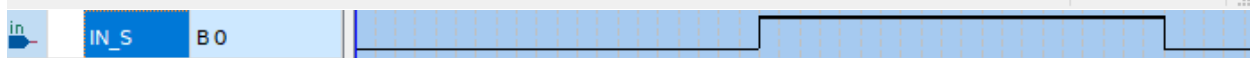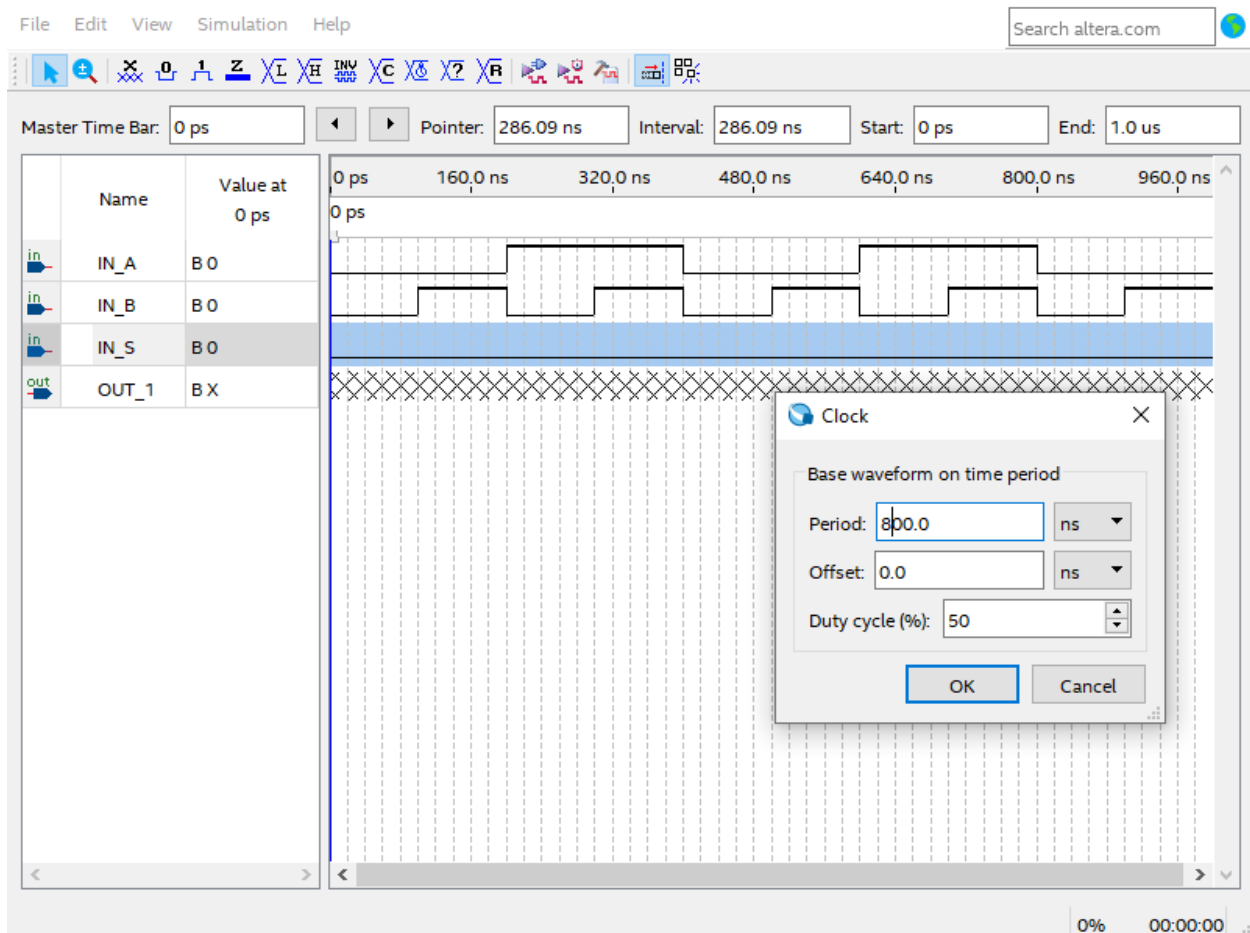
I repeat the same steps as above for IN_B but instead of 400ns, I do 200ns.



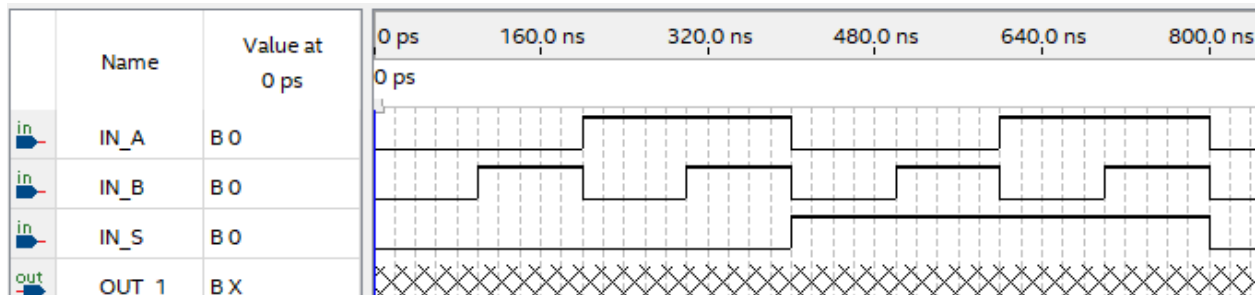
I repeat the same step again for IN_S but with 800ns.



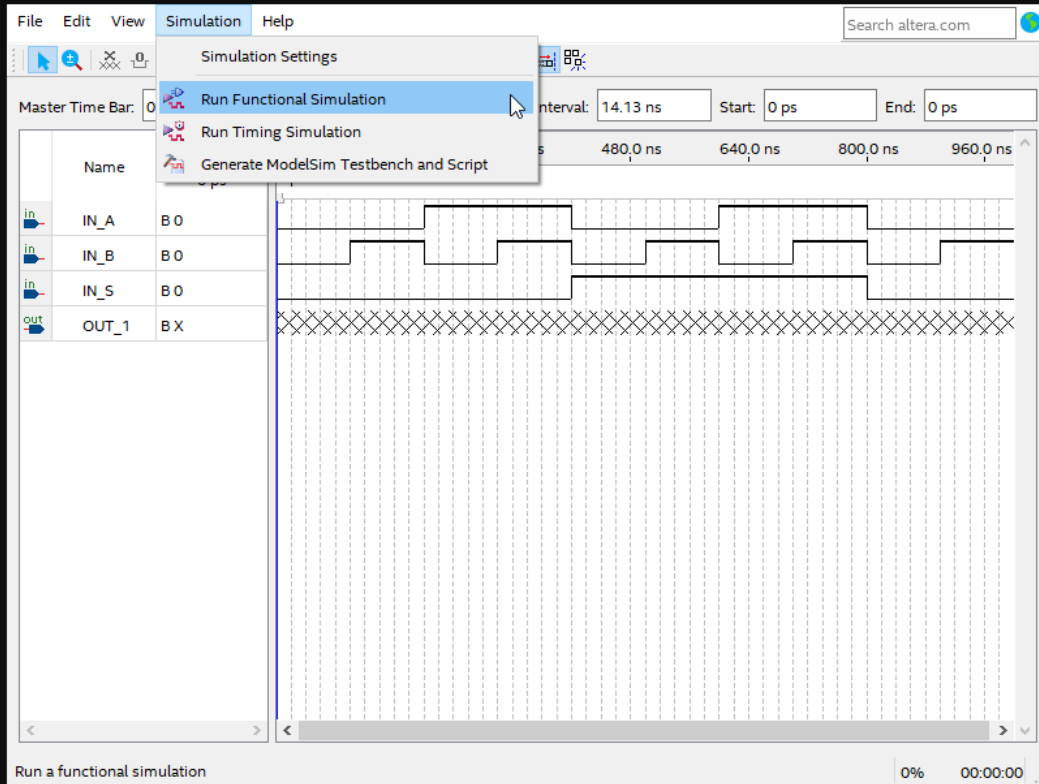My WVF now looks like this and I can begin the simulation



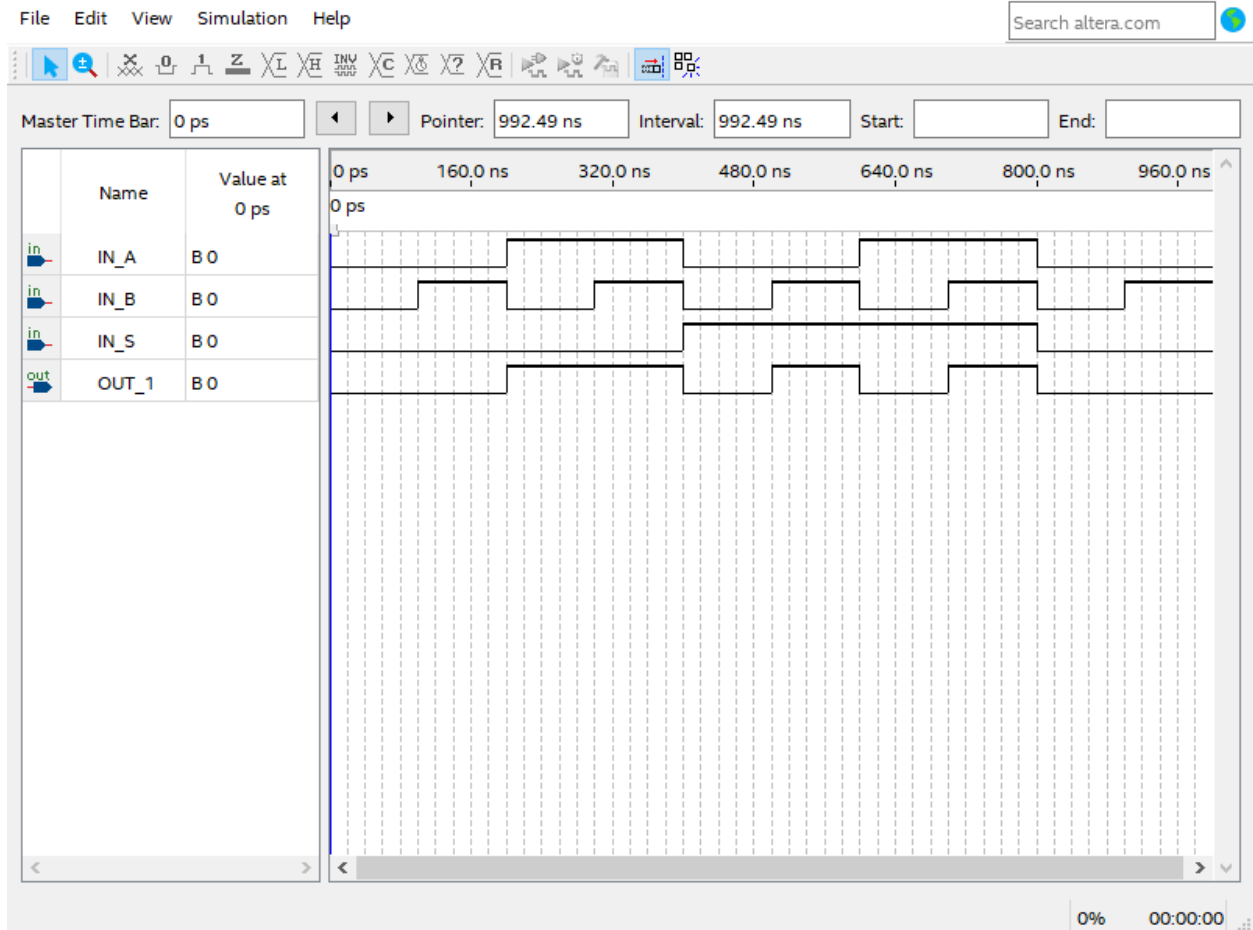I go to the simulation drop down and press run functional simulation



Afterwards, this should be the result. A WVF file with a proper line output instead of X's.

pins.txt - Notepad

File Edit Format View Help

To, Location



IN_A,PIN_AB12




IN_B,PIN_AC12

IN_S,PIN_AF9

Out_1,PIN_V16

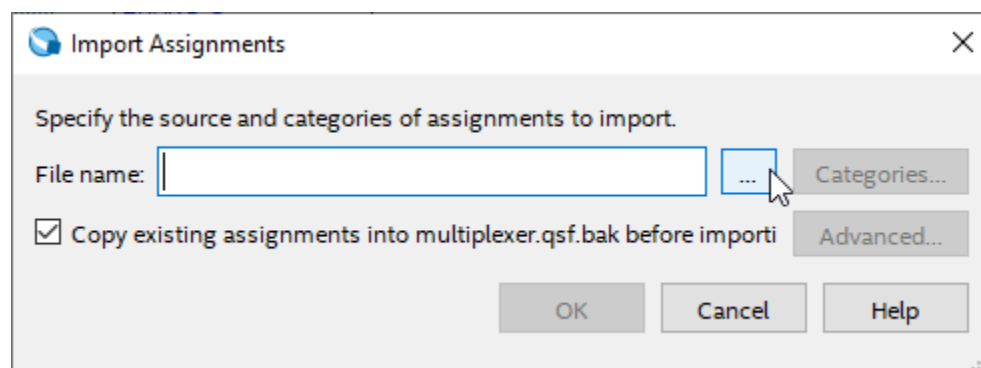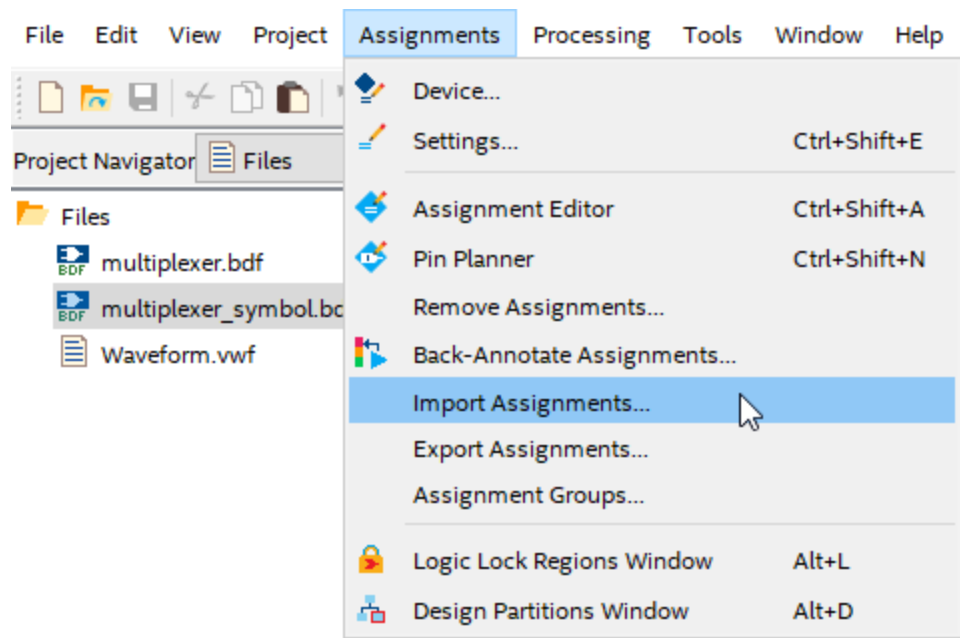
Next I create a text file with the naming convention "To, Location" where the To describes where the pin is assigned to and which pin to assign.



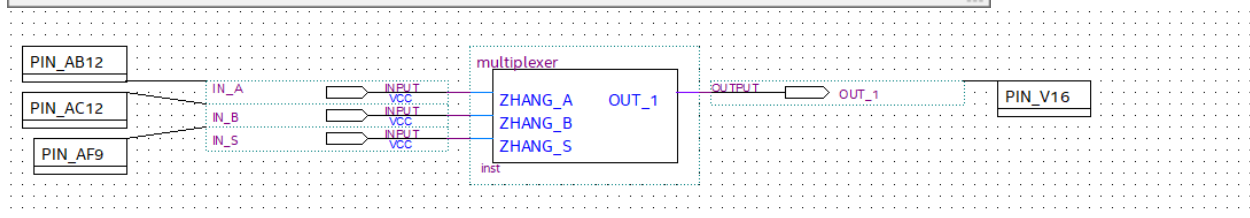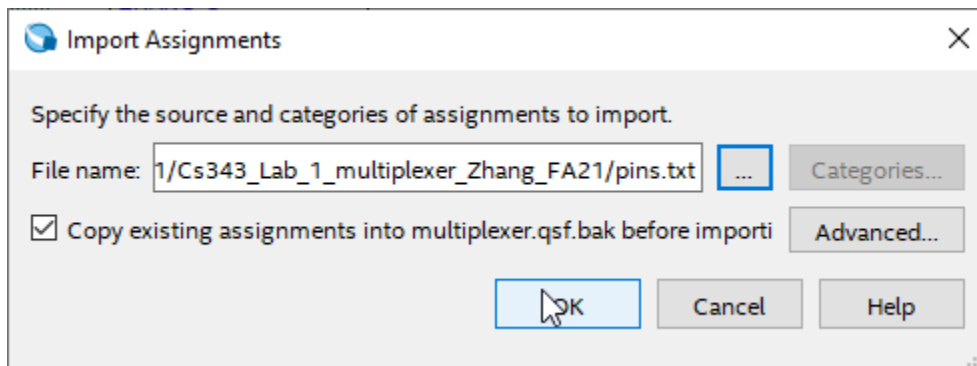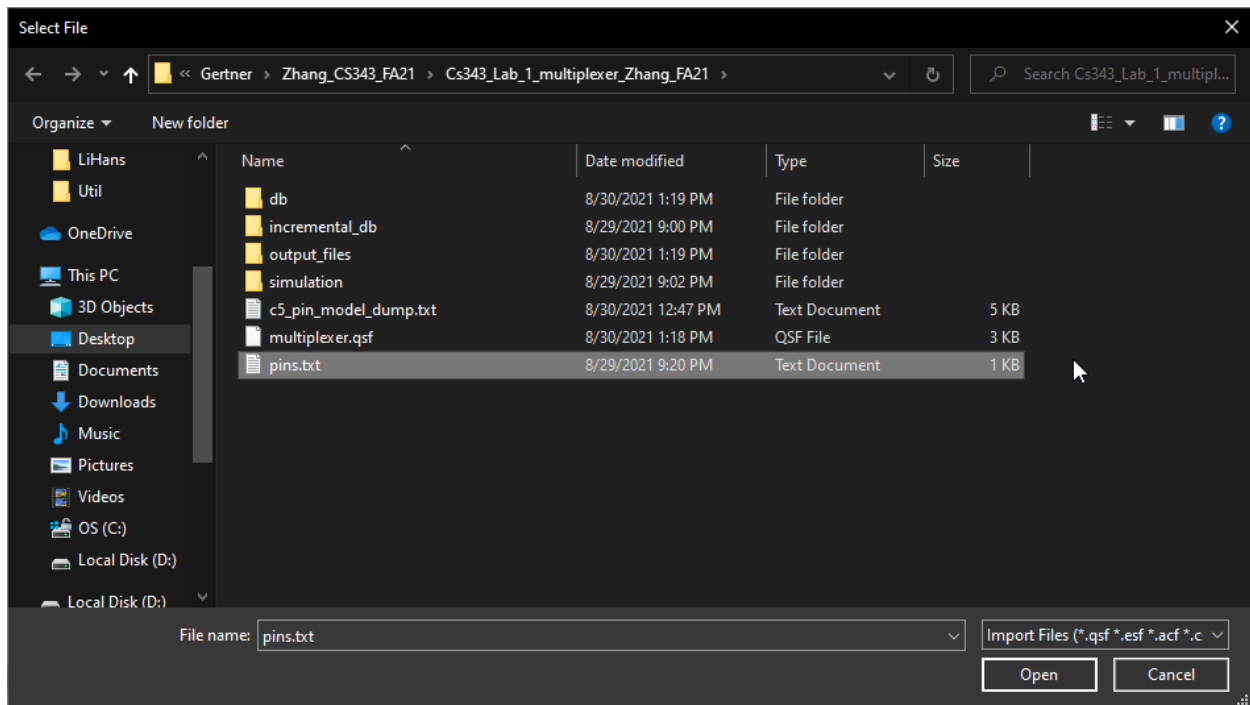


The next step is to go to the assignments and import assignments. Then press the ... when the popup shows which should allow you to select a file. Select the pins files that was created before and the output should show in the design file.


Task 3

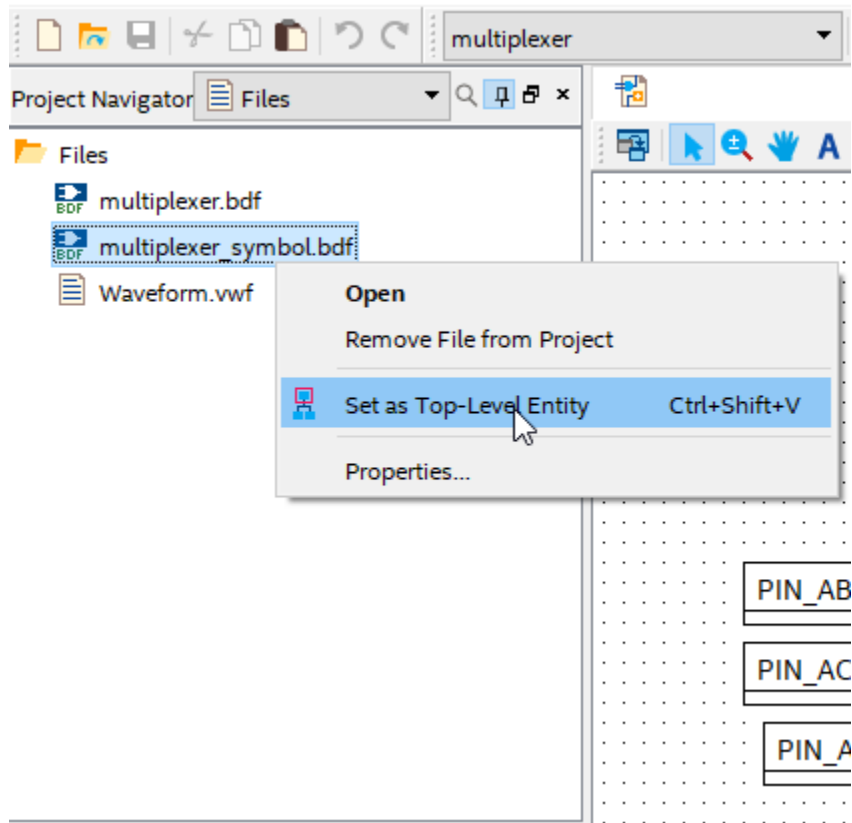

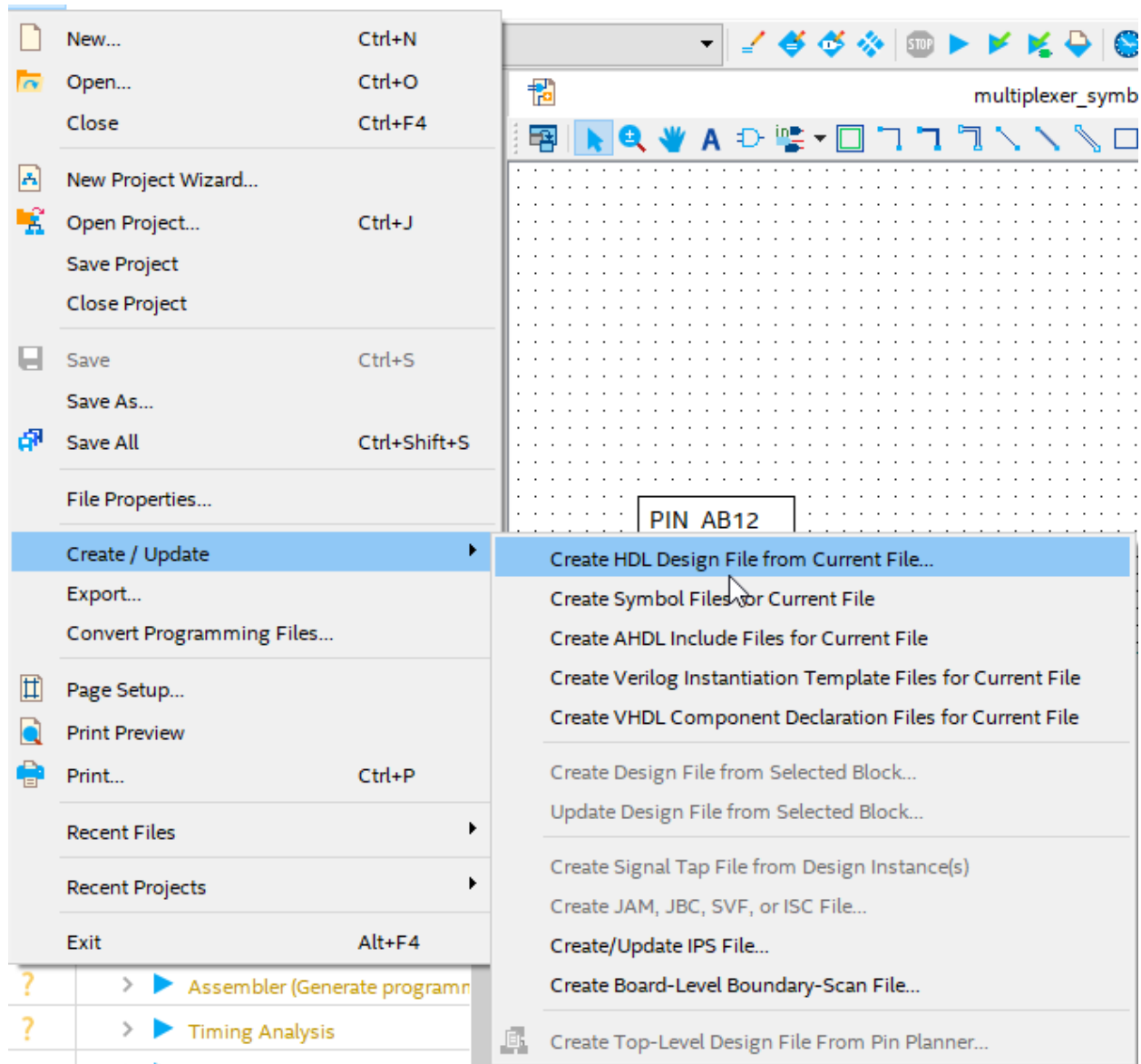It is important to set the correct top level entity, in my case it is the `multiplexer_symbol.bdf` which is basically the MUX as a symbol.



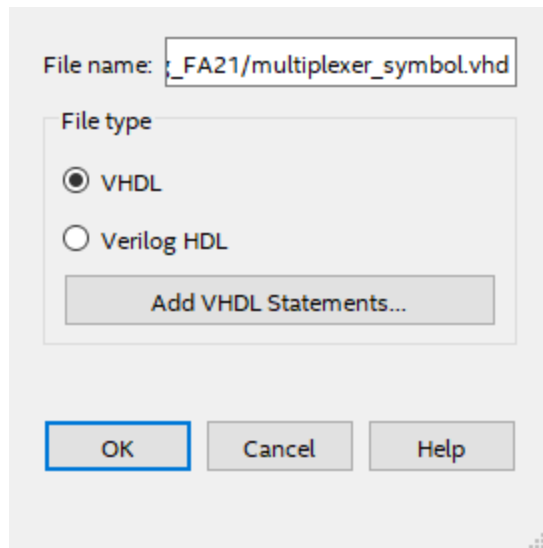Next go to files -> create/Update -> create HDL Design File from Current File...



A popup should show looking like this. Make sure the file type is in VHDL and not Verilog HDL

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

LIBRARY work;

ENTITY multiplexer_symbol IS
    PORT
    (
        IN_A : IN  STD_LOGIC;
        IN_B : IN  STD_LOGIC;
        IN_S : IN  STD_LOGIC;
        OUT_1 : OUT STD_LOGIC
    );
END multiplexer_symbol;

ARCHITECTURE bdf_type OF multiplexer_symbol IS

    COMPONENT multiplexer
        PORT(ZHANG_A : IN STD_LOGIC;
            ZHANG_B : IN STD_LOGIC;
            ZHANG_S : IN STD_LOGIC;
            OUT_1 : OUT STD_LOGIC
        );
    END COMPONENT;

BEGIN

    b2v_inst : multiplexer
    PORT MAP(ZHANG_A => IN_A,
            ZHANG_B => IN_B,
            ZHANG_S => IN_S,
            OUT_1 => OUT_1);

END bdf_type;

```

A vhd file should be generated now in your directory. Go into your directory and open the vhd file. I chose to use notepad to observe my vhd code.